

## Using Microchip's Micropower LDOs

Author: Paul Paglia,  
 Microchip Technology Inc.

### INTRODUCTION

Microchip Technology, Inc.'s family of micropower LDOs utilizes low-voltage CMOS process technology. These LDOs provide similar ripple rejection and drop-out characteristics as their bipolar equivalents, but are significantly more efficient. A typical bipolar regulator has base current equal to 1-2% of the output load, whereas Microchip's LDOs have approximately 60  $\mu\text{A}$  resulting in total operating current orders of magnitude lower than their bipolar counterparts. In addition, Microchip's LDOs can be placed in a shutdown mode, further enhancing their effectiveness in low-power applications.

This low-power operation makes Microchip's family of LDOs ideal for upgrading the LP2980 and MIC5205 bipolar LDOs in cellular phones, pagers, PDAs, laptops, hand-held meters, and other portable applications.

Microchip's micropower LDOs are available with fixed and adjustable outputs, supporting load currents up to 50 mA, 100 mA, 150 mA and 300 mA. SOT-23-5, SOT-23-6, SOT-223, and MSOP-8 packaging require minimal board space. Shutdown capability, thermal protection, and current limiting are standard in every device. Adjustable output, error flag, and noise bypass capability are provided on select devices (see Table 3).

### APPLICATIONS

#### Optimizing Output Voltage Accuracy of TC1070/TC1071 Adjustable LDOs


Microchip's LDOs are available in both adjustable and fixed output voltage options. The accuracy of the output depends on the initial accuracy, stability, and temperature coefficient of the internal bandgap reference and the feedback resistors.

Rather than specifying  $V_{OUT}$  accuracy on adjustable regulators, the initial accuracy and temperature coefficient of the internal reference is specified.  $V_{OUT}$  accuracy is not specified because it depends on the external feedback resistors. Figure 1 shows a typical adjustable LDO feedback circuit in which resistors  $R_1$  and  $R_2$  set the output voltage per the following formula:

#### EQUATION 1:

$$V_{OUT} = V_{REF}[(R_1/R_2) + 1]$$

$$V_{REF} = 1.20\text{V}$$

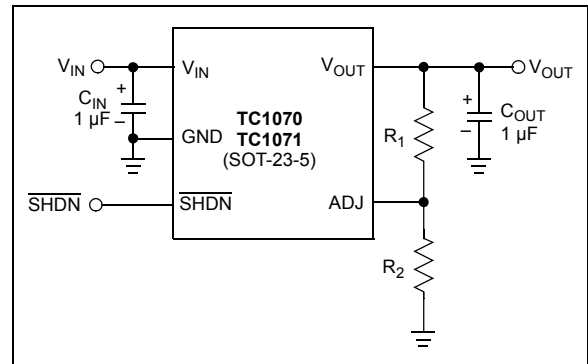

**FIGURE 1:** Adjustable LDO Feedback Circuit.

The ADJ pin is a high impedance CMOS input. Consequently, resistor values can be between 300 k $\Omega$  and 1 M $\Omega$  to minimize the current through  $R_1$  and  $R_2$ .

Inspection of Equation 1 reveals the following:

1. When  $V_{OUT}$  is made equal to  $V_{REF}$  (i.e.,  $R_1$  is zero), the tolerance of  $V_{OUT}$  will be approximately that of  $V_{REF}$ .
2. The tolerance of  $V_{OUT}$  is a function of both the tolerance of  $V_{REF}$  and the tolerance of the  $R_1/R_2$  ratio when  $V_{OUT}$  is greater than  $V_{REF}$  (i.e., when  $R_1/R_2 > 0$ ).

For the purposes of worst case analysis, the tolerances of  $R_1$  and  $R_2$  are additive. For example, if  $R_1$  and  $R_2$  are both 1% resistors, the maximum tolerance of the  $R_1/R_2$  ratio is 2%.

Re-examining the effect of tolerances on Equation 1 reveals that the tolerance of  $V_{OUT}$  worsens proportionally as the  $V_{OUT}$  setting departs the value of  $V_{REF}$ . Stated another way:

#### EQUATION 2:

$$ERROR_{V_{OUT}} \propto (V_{OUT} - V_{REF})$$

Table 1 shows that percentage of total output voltage error contributed by the tolerances of  $V_{REF}$  and  $R_1/R_2$  for various values of  $V_{OUT}$ .

# AN765

**TABLE 1: OUTPUT ERROR CONTRIBUTORS**

V <sub>OUT</sub> (V)	Reference Tolerance (%)	Resistor Tolerance (%)	Resistor Error (%)	Total Output Error (%)
1.23	2	1	0	2
1.23	2	2	0	2
2.0	2	1	0.77	2.77
2.0	2	2	1.54	3.54
2.46	2	1	1.0	3.0
2.46	2	2	2.0	4.0
3.0	2	1	1.2	3.2
3.0	2	2	2.4	4.2
4.0	2	1	1.38	3.38
4.0	2	2	2.76	4.76
5.0	2	1	1.50	3.5
5.0	2	2	3.0	5.0

The output voltage accuracy of the adjustable regulator improves with tighter tolerance resistors. However, accuracy will be limited to ±2% due to the accuracy of the reference. Table 2 shows output voltage accuracy for the adjustable LDO using 1%, 0.5%, and 0.1% tolerance resistors.

**TABLE 2: RESISTOR TOLERANCE EFFECT ON V<sub>OUT</sub> ERROR**

V <sub>OUT</sub>	V <sub>OUT</sub> Error		
	1% Resistor Tol.	0.5% Resistor Tol.	0.1% Resistor Tol.
5.0V	3.5%	2.75%	2.15%
4.0V	3.38%	2.69%	2.14%
3.0V	3.2%	2.6%	2.12%
2.46V	3.0%	2.5%	2.10%
2.0V	2.77%	2.39%	2.08%
1.23V	2.0%	2.0%	2.0%

## Power-Saving Shutdown Mode

All of Microchip's micropower LDOs have a shutdown input that allows the user to digitally disconnect the load from the power source and send the regulator into a low-power "sleep" mode. The supply current is reduced from 50 µA, during normal operation, to 0.05 µA in shutdown.

The  $\overline{\text{SHDN}}$  pin input current is guaranteed to be no greater than 1 µA (an order of magnitude lower than bipolar counterparts).

Shutdown mode is activated when  $\overline{\text{SHDN}}$  is below  $0.2 \times V_{\text{IN}}$ . In this mode, the pass transistor is turned OFF, disconnecting the load from the power source.


Shutdown mode is disabled, allowing normal device operation, when the input is above  $0.4 \times V_{\text{IN}}$ . This  $V_{\text{IN}}$  is low enough to ensure that a control output from a 3.3V microcontroller, operating from four fully-charged NiCad/NiMH cells (6V), can enable the LDO. If not used,  $\overline{\text{SHDN}}$  should not be left floating, but rather connected to  $V_{\text{IN}}$ .

## Out-of-Regulation (ERROR) Flag

The TC1070/1/2/3 and TC1054/5 each have Error Flag outputs that are asserted when the LDO falls out of regulation by approximately -5%.


The  $\overline{\text{ERROR}}$  pin is an N-channel open-drain output that can sink up to 1 mA. However, larger value pull-up resistors should be selected so that energy loss through  $\overline{\text{ERROR}}$  is kept to a minimum.  $\overline{\text{ERROR}}$  must be pulled to any supply voltage less than 7V through a pull-up resistor.

$\overline{\text{ERROR}}$  output is valid for input voltages above 1V and undefined for voltages below 1V. As the output is transitioning between 0V and 1.0V during power up/down, the Error output may float momentarily to 1.0V. If 1.0V is high enough to be interpreted as a logic '1', the two-resistor network shown in Figure 2 may be used. This will ensure that  $\overline{\text{ERROR}}$  never will rise above 0.5V during invalid states. Keep in mind the maximum that Error output can be in its high state is  $V_{\text{OUT}}/2$ .

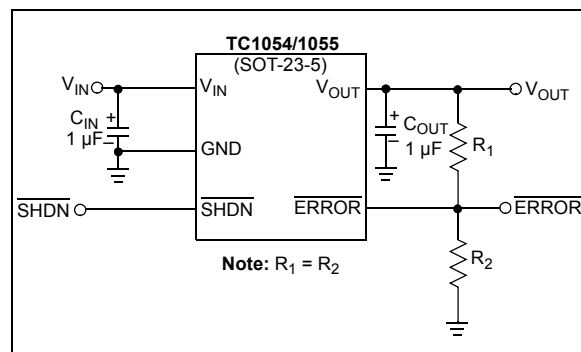

**FIGURE 2:** Ensuring Valid Error Output for Low V<sub>IN</sub> Levels.

By connecting an RC on  $\overline{\text{ERROR}}$  output, it can be used as a power on reset. During power up, the Error comparator will go high as soon as the regulator output is within tolerance.  $\overline{\text{ERROR}}$  will be delayed by the RC network before releasing the microcontroller from reset.

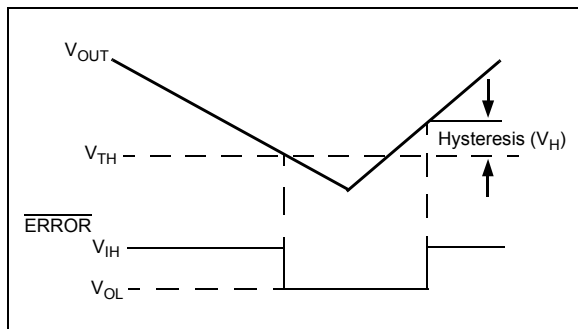

**FIGURE 3:** Out-of-Regulation Error Flag.

$\overline{\text{ERROR}}$  also can be used as a power quality monitor. If a low input voltage or an over-current condition causes the output to fall out of regulation,  $\overline{\text{ERROR}}$  will pull low, signifying an unstable power condition. This flags the microcontroller, which now can activate proper shutdown sequencing, ensuring orderly system operation.

The Error comparator has 50 mV of positive hysteresis to provide some  $V_{IN}$  noise immunity.

## Input, Output and Bypass Capacitors

It is recommended that input, output, and bypass capacitors be used for optimal device performance. To ensure stability in the LDO's feedback loop, a capacitor is required from the output to ground (Figures 4 and 5). Capacitors must be chosen that meet the ESR value range and minimum capacitance identified in device data sheets. In general, a 1  $\mu\text{F}$  - 2.2  $\mu\text{F}$  capacitor is recommended to ensure stable operation under maximum load conditions. Larger value capacitors (4.7  $\mu\text{F}$  to 10  $\mu\text{F}$ ) will increase transient load response and ripple rejection performance.

Ceramic capacitors offer the lowest ESR followed by, in order of increasing ESR, OS-CON, film, aluminum electrolytic, and tantalum. Film capacitors provide good performance, but usually are not a viable solution due to excessive cost and size. Ceramics combine excellent ESR with relatively small size. However, the ESR of ceramic capacitors sometimes can be too low, requiring a 1  $\Omega$  series resistor to ensure stability. OS-CON capacitors offer an ESR only slightly higher than ceramics, but consume more volume. The OS-CON capacitors exhibit rock-solid ESR from  $-55^\circ\text{C}$  to  $125^\circ\text{C}$ . Aluminum electrolytics are ideal for low-cost commercial temperature grade applications where board space is not a concern. Like OS-CON capacitors, electrolytics typically are offered in a radial lead package, but are

available in surface mount styles. Tantalums offer an ESR similar to aluminum electrolytics. They also provide a reasonable cost, high-volume efficiency solution and are usually the capacitor of choice.

A 1  $\mu\text{F}$  input capacitor should be installed from  $V_{CC}$  to GND (Figures 4 and 5) if the IC is powered from a battery or if there is excessive (>1 ft) distance between the regulator and the AC filter capacitor. A larger value capacitor will provide better  $V_{CC}$  noise rejection and improved performance when the supply has a high AC impedance. A 470 pf bypass capacitor can be tied to the bypass pin on the TC1014/1015 and TC1072/1073 or the ADJ pin on the TC1070/1071 (see Figure 5) to reduce the  $V_{REF}$  noise.

## Thermal Issues

The amount of power that the LDO dissipates is a function of the bias supply current and the pass-through current. The pass-through current is the current that flows from  $V_{CC}$  through the pass transistor of the LDO to the load. The following equation is used to calculate power dissipation:

### EQUATION 3:

$$P_D = (V_{CC} \times I_S) + [(V_{CC} - V_{OUT})I_{LOAD}]$$

Maximum values of  $V_{CC}$  and  $I_{LOAD}$  and minimum values for  $V_{OUT}$  should be used when calculating  $P_D$  to ensure worst-case conditions are met.

The amount of power that the LDO can dissipate depends on the ambient temperature ( $T_A$ ). A guard-banded maximum die temperature ( $T_{JMAX}$ ) of  $+125^\circ\text{C}$  is used to account for variations in thermal conductivity of PC boards and variations in airflow.

### EQUATION 4:

$$\theta_{JA} = (T_{JMAX} - T_A) / PD_{MAX}$$

$$\theta_{JA} = \theta_{JC} + \theta_{CA}$$

$\theta_{JC}$  is the thermal resistance from the die surface to the package body and leads.  $\theta_{CA}$  is the thermal resistance from the package body and leads to the surrounding air, PC board dielectric, and traces.

The SOT-23-5 and SOT-23-6 packages have a worst-case  $\theta_{JA}$  of  $220^\circ\text{C}/\text{W}$  when mounted on a single-layer FR4 dielectric copper-clad PC board. This  $\theta_{JA}$  can be reduced by using a PC board made with a dielectric that has a better heat transfer coefficient. Additionally, adding a ground plane and large supply traces to the IC will provide better thermal conductivity. The values for  $\theta_{JA}$  are for a system that uses natural convection. A significant reduction in  $\theta_{CA}$  can be induced with forced airflow.

# AN765


Given:

$$\theta_{JA} = 220^{\circ}\text{C/W}$$


$$\therefore P_{D\text{MAX}} = (125^{\circ}\text{C} - T_A) / 220^{\circ}\text{C/W}$$

Ambient Temperature	P <sub>D</sub> MAX
+25°C	0.454W
+50°C	0.341W
+85°C	0.182W

Excessive power dissipation will result in elevated die temperatures that could activate the device's thermal shutdown. The LDOs have an integrated thermal protection circuitry that disables the LDO when die temperatures exceed approximately +160°C. Ten degrees Celsius of hysteresis is built into the protection circuitry, such that the LDO is not released from thermal shutdown until the die temperature drops to +150°C. In addition to thermal protection, an internal sense resistor in series with the pass element provides a short-circuit limit.

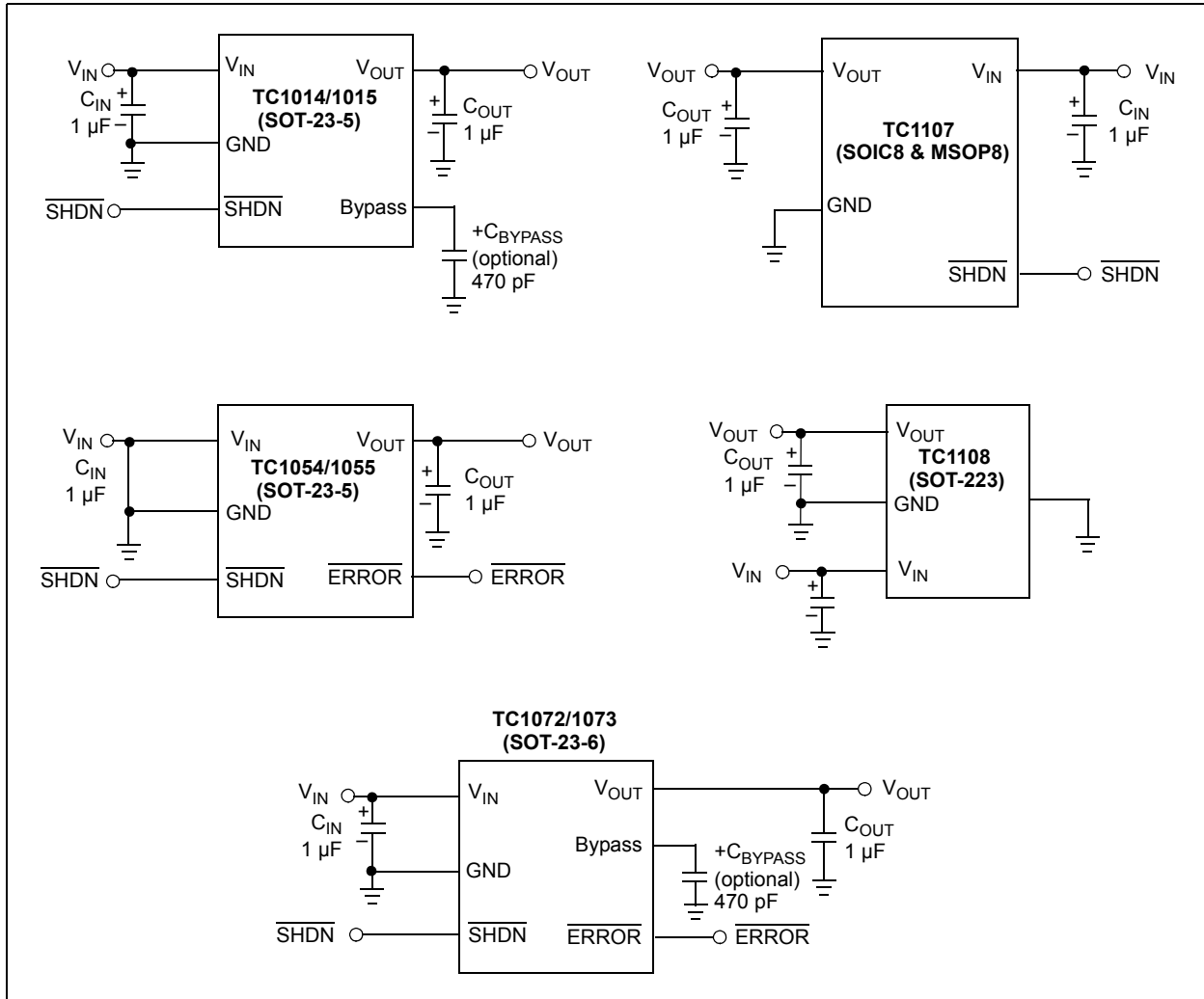

**FIGURE 4:** Typical Application Circuit (Fixed Output)

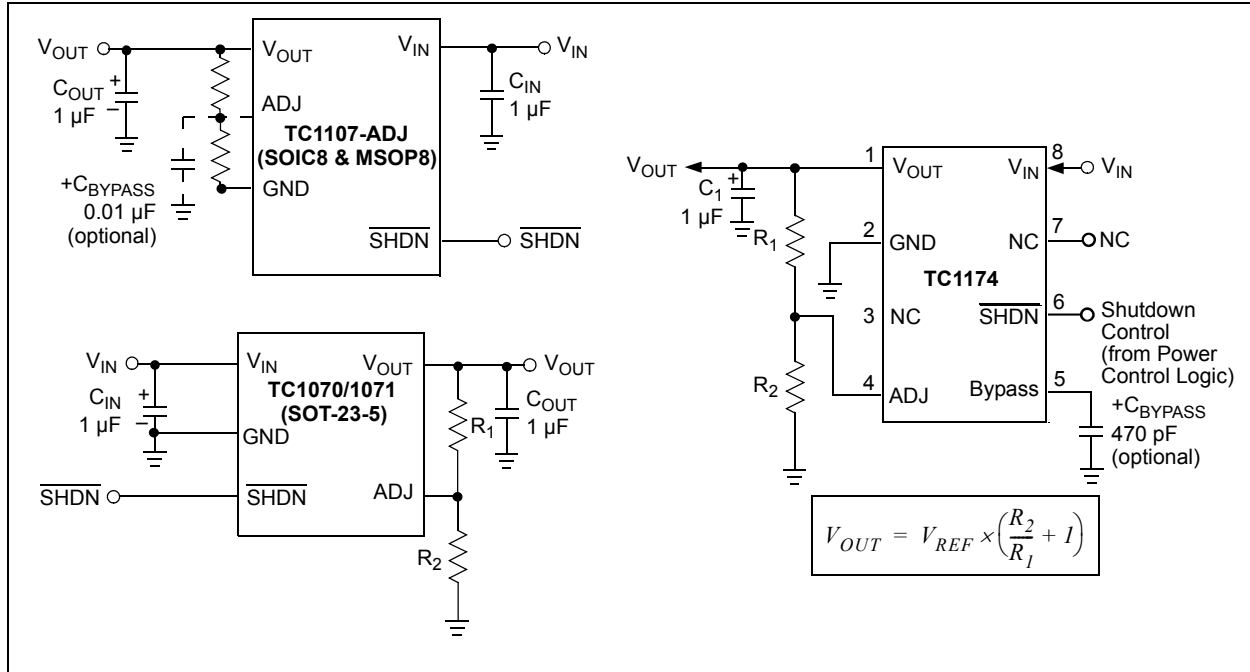

**FIGURE 5:** Typical Application Circuit (Adjustable Output).

**TABLE 3: CMOS LDOs SELECTION GUIDE**

Part No.	Package	Output Voltage †										ADJ	SHDN	Error Flag	Bypass	I <sub>SS</sub> Typ. (μA)	I <sub>OUT</sub> Max (mA)	V <sub>DROP</sub> Typ. (mV)	
		2.5V	2.7V	2.8V	2.84V	2.85V	3.0V	3.15V	3.3V	3.6V	4.0V								5.0V
TC1014	SOT-23-5	X	X			X	X		X	X	X	X	X	X			50	50	85
TC1015	SOT-23-5	X	X			X	X		X	X	X	X	X	X			50	100	180
TC1054	SOT-23-5	X	X			X	X		X	X	X	X	X	X	X		50	50	85
TC1055	SOT-23-5	X	X			X	X		X	X		X	X	X	X		50	100	180
TC1070	SOT-23-5													X	X		50	50	85
TC1071	SOT-23-5													X	X		50	100	180
TC1072	SOT-23-6	X	X			X	X		X	X	X	X	X	X		X	50	50	85
TC1073	SOT-23-6	X	X			X	X		X	X	X	X	X	X		X	50	100	180
TC1107	MSOP-8, SOIC-8			X		X			X			X	X	X		X	50	300	240
TC1108	SOT-223			X		X			X			X	X	X			50	300	240
TC1173	MSOP-8, SOIC-8			X		X			X			X	X	X	X		50	100	180
TC1174	MSOP-8, SOIC-8												X	X		X	50	300	240
TC1185	SOT-23-5	X	X			X	X		X	X	X	X	X	X		X	50	150	270
TC1186	SOT-23-5	X	X			X	X		X	X	X	X	X	X	X		50	150	270
TC1187	SOT-23-5												X	X	X		50	150	270
TC1188*	SOT-23-5			X	X			X						X			50	100	55
TC1189*	SOT-23-5			X	X			X						X			50	100	55
TC1223	SOT-23-5	X	X			X	X		X	X	X	X	X	X			50	50	85
TC1224	SOT-23-5	X	X			X	X		X	X	X	X	X	X			50	100	180

\* Pin Compatible Replacement for MAX8863/8864.

† Custom Output Voltages Available - Contact Microchip Technology.

# AN765

---

NOTES:

---

**Note the following details of the code protection feature on Microchip devices:**

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable.”

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

---

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

**Trademarks**

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KEELOQ, KEELOQ logo, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, PowerSmart, rPIC, and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AmpLab, FilterLab, Linear Active Thermistor, Migratable Memory, MXDEV, MXLAB, PS logo, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, PICkit, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, REAL ICE, rLAB, rfPICDEM, Select Mode, Smart Serial, SmartTel, Total Endurance, UNI/O, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2007, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

*Microchip received ISO/TS-16949:2002 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona, Gresham, Oregon and Mountain View, California. The Company's quality system processes and procedures are for its PIC<sup>®</sup> MCUs and dsPIC<sup>®</sup> DSCs, KEELOQ<sup>®</sup> code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.*

**QUALITY MANAGEMENT SYSTEM  
CERTIFIED BY DNV  
== ISO/TS 16949:2002 ==**



## WORLDWIDE SALES AND SERVICE

### AMERICAS

**Corporate Office**  
2355 West Chandler Blvd.  
Chandler, AZ 85224-6199  
Tel: 480-792-7200  
Fax: 480-792-7277  
Technical Support:  
http://support.microchip.com  
Web Address:  
www.microchip.com

**Atlanta**  
Duluth, GA  
Tel: 678-957-9614  
Fax: 678-957-1455

**Boston**  
Westborough, MA  
Tel: 774-760-0087  
Fax: 774-760-0088

**Chicago**  
Itasca, IL  
Tel: 630-285-0071  
Fax: 630-285-0075

**Dallas**  
Addison, TX  
Tel: 972-818-7423  
Fax: 972-818-2924

**Detroit**  
Farmington Hills, MI  
Tel: 248-538-2250  
Fax: 248-538-2260

**Kokomo**  
Kokomo, IN  
Tel: 765-864-8360  
Fax: 765-864-8387

**Los Angeles**  
Mission Viejo, CA  
Tel: 949-462-9523  
Fax: 949-462-9608

**Santa Clara**  
Santa Clara, CA  
Tel: 408-961-6444  
Fax: 408-961-6445

**Toronto**  
Mississauga, Ontario,  
Canada  
Tel: 905-673-0699  
Fax: 905-673-6509

### ASIA/PACIFIC

**Asia Pacific Office**  
Suites 3707-14, 37th Floor  
Tower 6, The Gateway  
Harbour City, Kowloon  
Hong Kong  
Tel: 852-2401-1200  
Fax: 852-2401-3431

**Australia - Sydney**  
Tel: 61-2-9868-6733  
Fax: 61-2-9868-6755

**China - Beijing**  
Tel: 86-10-8528-2100  
Fax: 86-10-8528-2104

**China - Chengdu**  
Tel: 86-28-8665-5511  
Fax: 86-28-8665-7889

**China - Fuzhou**  
Tel: 86-591-8750-3506  
Fax: 86-591-8750-3521

**China - Hong Kong SAR**  
Tel: 852-2401-1200  
Fax: 852-2401-3431

**China - Qingdao**  
Tel: 86-532-8502-7355  
Fax: 86-532-8502-7205

**China - Shanghai**  
Tel: 86-21-5407-5533  
Fax: 86-21-5407-5066

**China - Shenyang**  
Tel: 86-24-2334-2829  
Fax: 86-24-2334-2393

**China - Shenzhen**  
Tel: 86-755-8203-2660  
Fax: 86-755-8203-1760

**China - Shunde**  
Tel: 86-757-2839-5507  
Fax: 86-757-2839-5571

**China - Wuhan**  
Tel: 86-27-5980-5300  
Fax: 86-27-5980-5118

**China - Xian**  
Tel: 86-29-8833-7250  
Fax: 86-29-8833-7256

### ASIA/PACIFIC

**India - Bangalore**  
Tel: 91-80-4182-8400  
Fax: 91-80-4182-8422

**India - New Delhi**  
Tel: 91-11-4160-8631  
Fax: 91-11-4160-8632

**India - Pune**  
Tel: 91-20-2566-1512  
Fax: 91-20-2566-1513

**Japan - Yokohama**  
Tel: 81-45-471-6166  
Fax: 81-45-471-6122

**Korea - Gumi**  
Tel: 82-54-473-4301  
Fax: 82-54-473-4302

**Korea - Seoul**  
Tel: 82-2-554-7200  
Fax: 82-2-558-5932 or  
82-2-558-5934

**Malaysia - Penang**  
Tel: 60-4-646-8870  
Fax: 60-4-646-5086

**Philippines - Manila**  
Tel: 63-2-634-9065  
Fax: 63-2-634-9069

**Singapore**  
Tel: 65-6334-8870  
Fax: 65-6334-8850

**Taiwan - Hsin Chu**  
Tel: 886-3-572-9526  
Fax: 886-3-572-6459

**Taiwan - Kaohsiung**  
Tel: 886-7-536-4818  
Fax: 886-7-536-4803

**Taiwan - Taipei**  
Tel: 886-2-2500-6610  
Fax: 886-2-2508-0102

**Thailand - Bangkok**  
Tel: 66-2-694-1351  
Fax: 66-2-694-1350

### EUROPE

**Austria - Wels**  
Tel: 43-7242-2244-39  
Fax: 43-7242-2244-393

**Denmark - Copenhagen**  
Tel: 45-4450-2828  
Fax: 45-4485-2829

**France - Paris**  
Tel: 33-1-69-53-63-20  
Fax: 33-1-69-30-90-79

**Germany - Munich**  
Tel: 49-89-627-144-0  
Fax: 49-89-627-144-44

**Italy - Milan**  
Tel: 39-0331-742611  
Fax: 39-0331-466781

**Netherlands - Drunen**  
Tel: 31-416-690399  
Fax: 31-416-690340

**Spain - Madrid**  
Tel: 34-91-708-08-90  
Fax: 34-91-708-08-91

**UK - Wokingham**  
Tel: 44-118-921-5869  
Fax: 44-118-921-5820